



COLLEGE OF ENGINEERING  
SCHOOL OF AEROSPACE ENGINEERING

AE 6705: INTRODUCTION TO MECHATRONICS

---

# LAB1

---

*Professor:*

Jonathan Rogers  
Gtech AE Professor

*Student:*

Tomoki Koike  
Gtech MS Student

September 4, 2021

## Table of Contents

|   |            |   |
|---|------------|---|
| 1 | Question 1 | 2 |
| 2 | Question 2 | 2 |
| 3 | Question 3 | 2 |
| 4 | Question 4 | 3 |

## Question 1

---

### Solution:

We are given that

$$R_f = 4k\Omega, \quad R_g = 1k\Omega.$$

We also know that the resistance of the resistor at the non-inverting terminal is computed as the equivalent resistance of the parallel combination of resistors involved in the feedback path ( $R - f$  and  $R_g$ ). Thus,

$$\begin{aligned}\frac{1}{R_{in}} &= \frac{1}{R_f} + \frac{1}{R_g} \\ \frac{1}{R_{in}} &= \frac{1}{4000} + \frac{1}{1000} \\ \frac{1}{R_{in}} &= \frac{5}{4000}\end{aligned}$$

Hence,

$R_{in} = 800\Omega$

## Question 2

---

### Solution:

Let one of the resistors have the resistance of  $R_1 = 700\Omega$ . With the formula for the voltage divider we can compute the other resistance,  $R_2$  to be

$$\begin{aligned}5 &= \frac{R_2}{700 + R_2} 12 \\ 5R_2 + 3500 &= 12R_2 \\ 7R_2 &= 3500\end{aligned}$$

Hence,

$R_1 = 700\Omega, \quad R_2 = 500\Omega$

## Question 3

---

**Solution:**

If  $R_g = 1k\Omega$  and if the sensor amplifier requires a gain of 10, we can compute the other resistance,  $R_f$  in the following way.

$$\begin{aligned}10 &= 1 + \frac{R_f}{R_g} \\10 &= 1 + \frac{R_f}{1000} \\ \frac{R_f}{1000} &= 9\end{aligned}$$

Hence,

$$R_g = 1k\Omega, \quad R_f = 9k\Omega$$

## Question 4

---

**Solution:**

The temperature sensor is designed to have  $10mV/^{\circ}F$ . If  $0.4V$  corresponds to  $10^{\circ}F$  which is an output of  $100mV$  from the sensor, we can compute the gain to be

$$G = 4.$$

If the MCU reads the voltage in the range of  $400mV$  to  $5V$ , we can tell that the range for the sensor's voltage output will be the range divided by the gain of 4. Hence, the range of  $100mV$  to  $1025mV$ . Since the sensor reads  $10mV/^{\circ}F$ , we know that the temperature range that can be measured by the MCU is

$$10^{\circ}F \text{ to } 102.5^{\circ}F.$$