

GIVEN

10V battery supply, constant current 0.5 A
to a resistor (R) for 30 min

FIND

(a) resistance R

(b) Energy transfer by work in kJ

EQUATION

$$V = IR$$

$$P = VI$$

$$W = Pt$$


$$P = \text{power}$$

$$t = \text{time}$$

$$W = \text{work}$$

ASSUMPTION

closed system

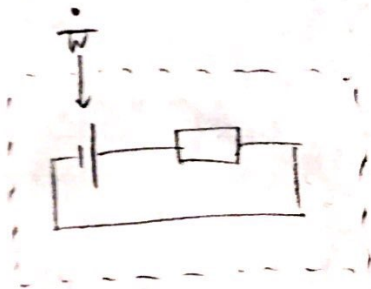FEEDSOLN

$$(a) R = \frac{V}{I} = \frac{10V}{0.5A} = \boxed{20 \Omega}$$

$$(b) W = (60 \times 30 s)(10V)(0.5A) \\ = 9000 J \\ = \boxed{9 \text{ kJ}}$$